

Core Equation (Series Resistance): $R_{\text{total}} = R_1 + R_2 + \dots$ **Variables & Units:** R_{total} = Total resistance (_____, Ohms) R_1, R_2 = Individual resistances (_____, Ohms)**Related Equations:** $V = I \times R$ | $P = I \times V$ | $P = I^2 \times R$ | $P = \frac{V^2}{R}$ **Section A: Formula Recall & Unit Conversions**1. The formula for total resistance in a series circuit is $R_{\text{total}} = R_1 + R_2$.a) Rearrange the formula to make R_1 the subject.

b) Rearrange the formula to make R_2 the subject.

2. Complete the following unit conversions. Show your working where appropriate.

a) $2.5 \text{ k}\Omega = \text{_____} \Omega$ b) $0.015 \text{ M}\Omega = \text{_____} \Omega$ c) $470 \Omega = \text{_____} \text{ k}\Omega$ d) $120000 \Omega = \text{_____} \text{ M}\Omega$ e) $50 \text{ mA} = \text{_____} \text{ A}$ f) $0.25 \text{ A} = \text{_____} \text{ mA}$ **Section B: Series Resistance Calculations**

For all questions in this section, assume the resistors are connected in series. Show all your working.

1. A circuit contains two resistors, $R_1 = 15 \Omega$ and $R_2 = 25 \Omega$.

a) Calculate the total resistance of the circuit.

b) If a third resistor, $R_3 = 10 \Omega$, is added in series, what is the new total resistance?

2. A series circuit has a total resistance of 120Ω . One of the resistors, R_A , has a resistance of 75Ω .a) Calculate the resistance of the other resistor, R_B .

- b) If the circuit is connected to a 6.0 V power supply, calculate the current flowing through R_A .

Section C: Application & Multi-step Problems

Figure 1 shows a simple series circuit containing a cell, a fixed resistor (R_F), and a thermistor (R_T).

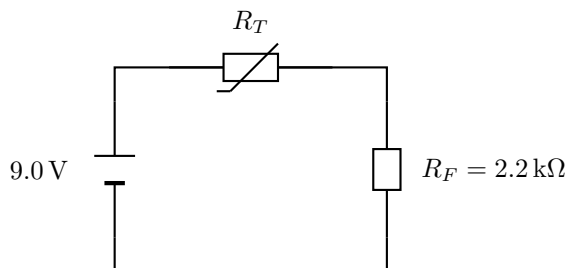


Figure 1: Thermistor Sensing Circuit

1. At a specific temperature, the thermistor (R_T) has a resistance of $1.8\text{ k}\Omega$. The fixed resistor (R_F) has a resistance of $2.2\text{ k}\Omega$.

- a) Calculate the total resistance of the circuit in Ohms.

- b) Calculate the current flowing through the circuit. Give your answer in milliamperes (mA) to an appropriate number of significant figures.

2. The circuit is used as a temperature sensor. The resistance of an NTC thermistor decreases as temperature increases.

- a) Explain how an increase in temperature affects the total resistance of the circuit and the current flowing through it.

- b) Calculate the power dissipated by the fixed resistor (R_F) when the current flowing through the circuit is 2.5 mA . Give your answer in milliwatts (mW).
